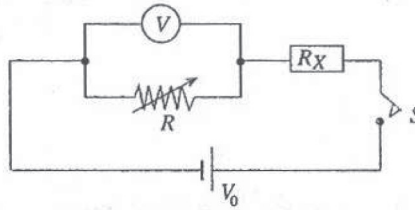


2011 A/L Structured Essay Question No (04)

4.



A student is asked to find the value R_x of an unknown resistor connected to the circuit shown, using a graphical method. R is a variable resistance provided by a resistance box. V is the reading of the voltmeter connected across R . The internal resistance of the voltmeter is large. Two new dry cells of voltage 1.5 V each is used to provide a voltage V_0 of 3 V. Assume that the internal resistance of such a dry cell battery is negligible.

- (a) Indicate the polarity of the voltmeter by labeling its terminals with + and - signs.
- (b) In order to plot a graph, the student is asked to take several voltmeter readings (V) by varying the resistance R .

(i) Write down an expression relating V , R , V_0 and R_x .

.....

.....

.....


(ii) Rearrange the variables in order to plot a straight line graph with $\frac{1}{V}$ on the Y axis.

.....

.....

.....

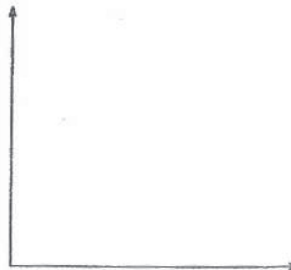(iii) Draw a rough sketch of the expected curve. Label the axes.



(iv) How would you find the value of R_x from the graph?

.....

.....

(v) How would you find the voltage V_0 of the battery using the graph?

.....

(c) You are given that the internal resistance of the voltmeter is $1500\ \Omega$ and the value of R_x is of the order of $100\ \Omega$. Of the following ranges given, indicate with a tick (\checkmark) the range of values that you would choose for R in order to obtain the straight line graph.

$25\ \Omega - 500\ \Omega$ (.....)

$25\ \Omega - 1500\ \Omega$ (.....)

$25\ \Omega - 2000\ \Omega$ (.....)

Give the reason for your choice.

.....
.....

(d) (i) How would you check experimentally whether the data have been affected by the possible run-down of the battery?

.....

(ii) If you have discovered that the battery has run-down, how would you design another battery which lasts longer time, using new $1.5\ \text{V}$ cells to give $3\ \text{V}$, before repeating the experiment. (If necessary you may also draw a diagram to illustrate the answer.)

.....
.....
.....